Write the missing words. Use the word bank.

Name _____ Date _____

Light Bulb Electrical Circuit

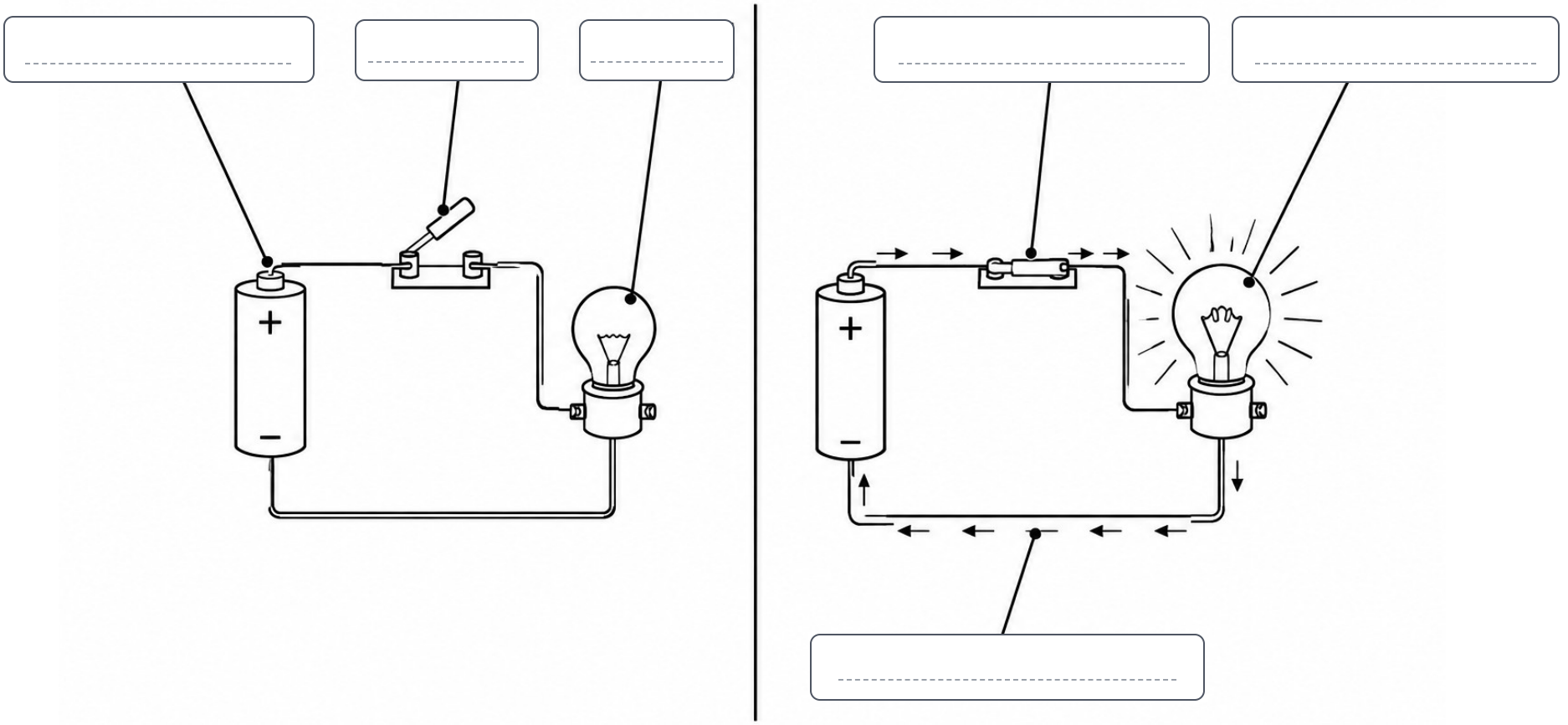

WORD BANK Unlit Bulb • Glowing Bulb • Open Switch • Closed Switch • Battery • Electric Current

Light Bulb Electrical Circuit

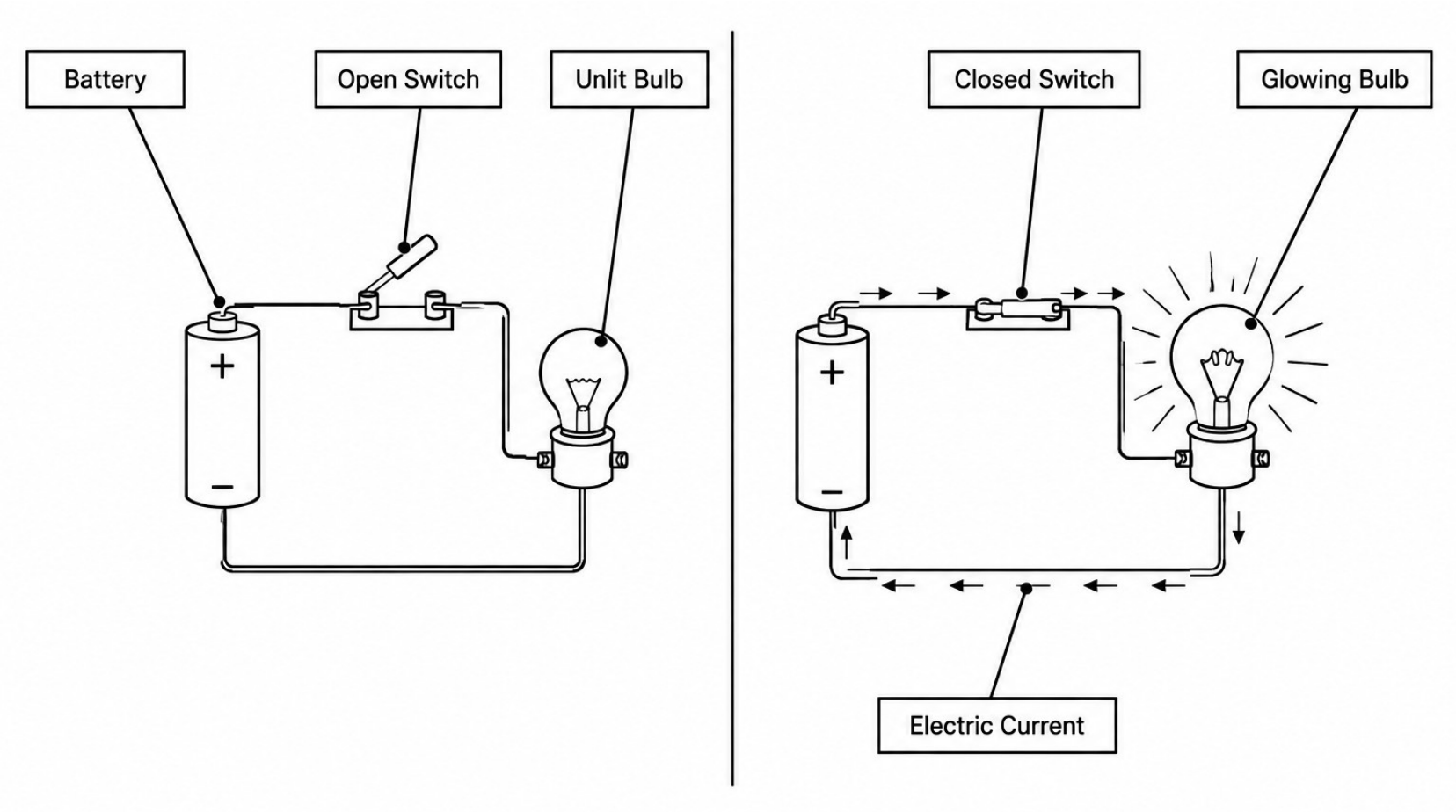

Light Bulb Electrical Circuit

