
Write the missing words. Use the word bank.


Name _____ Date _____

Complete Electrical Circuit

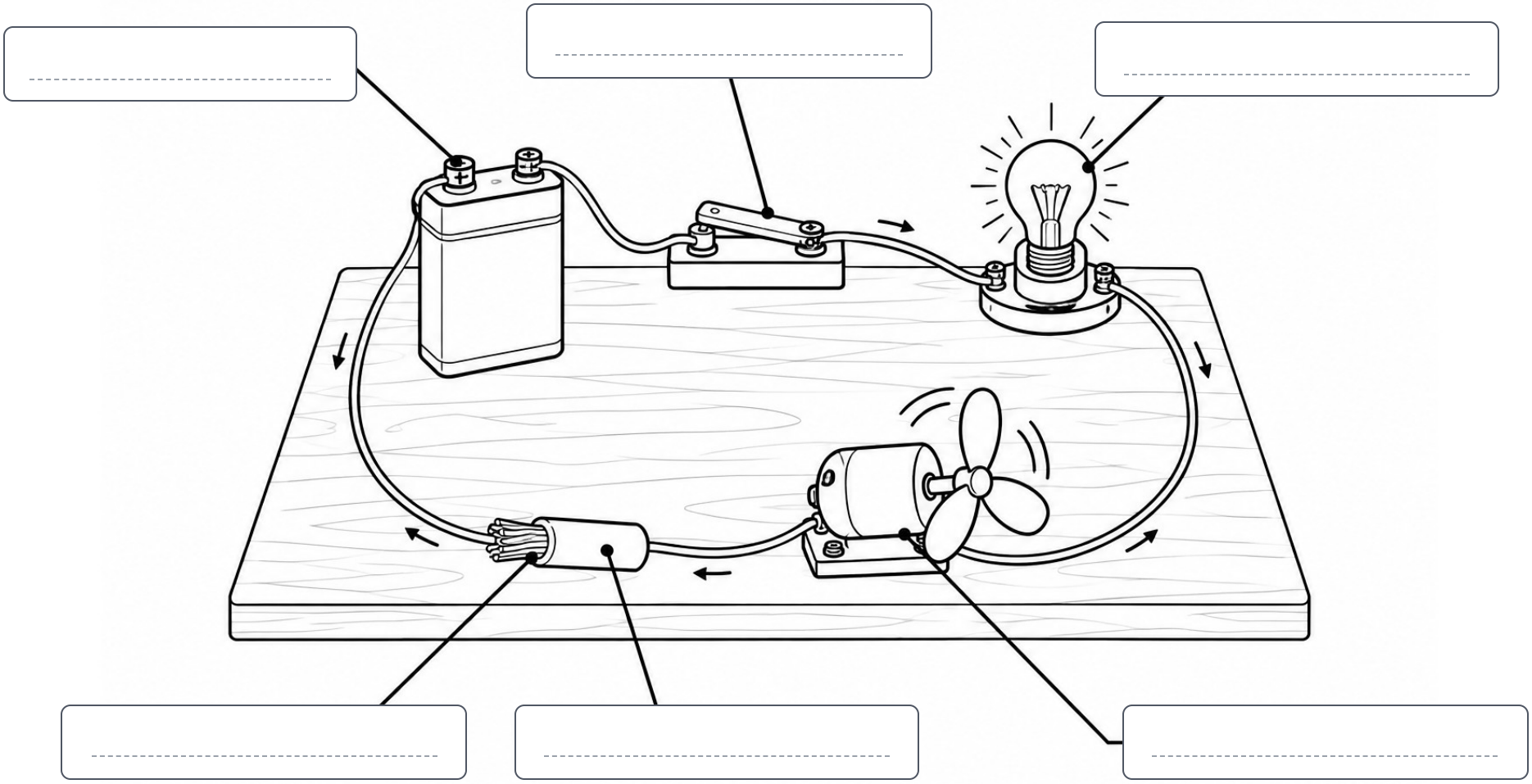

WORD BANK Copper Wire • Plastic Insulator • Electric Motor • Light Bulb • Closed Switch • Battery

Complete Electrical Circuit

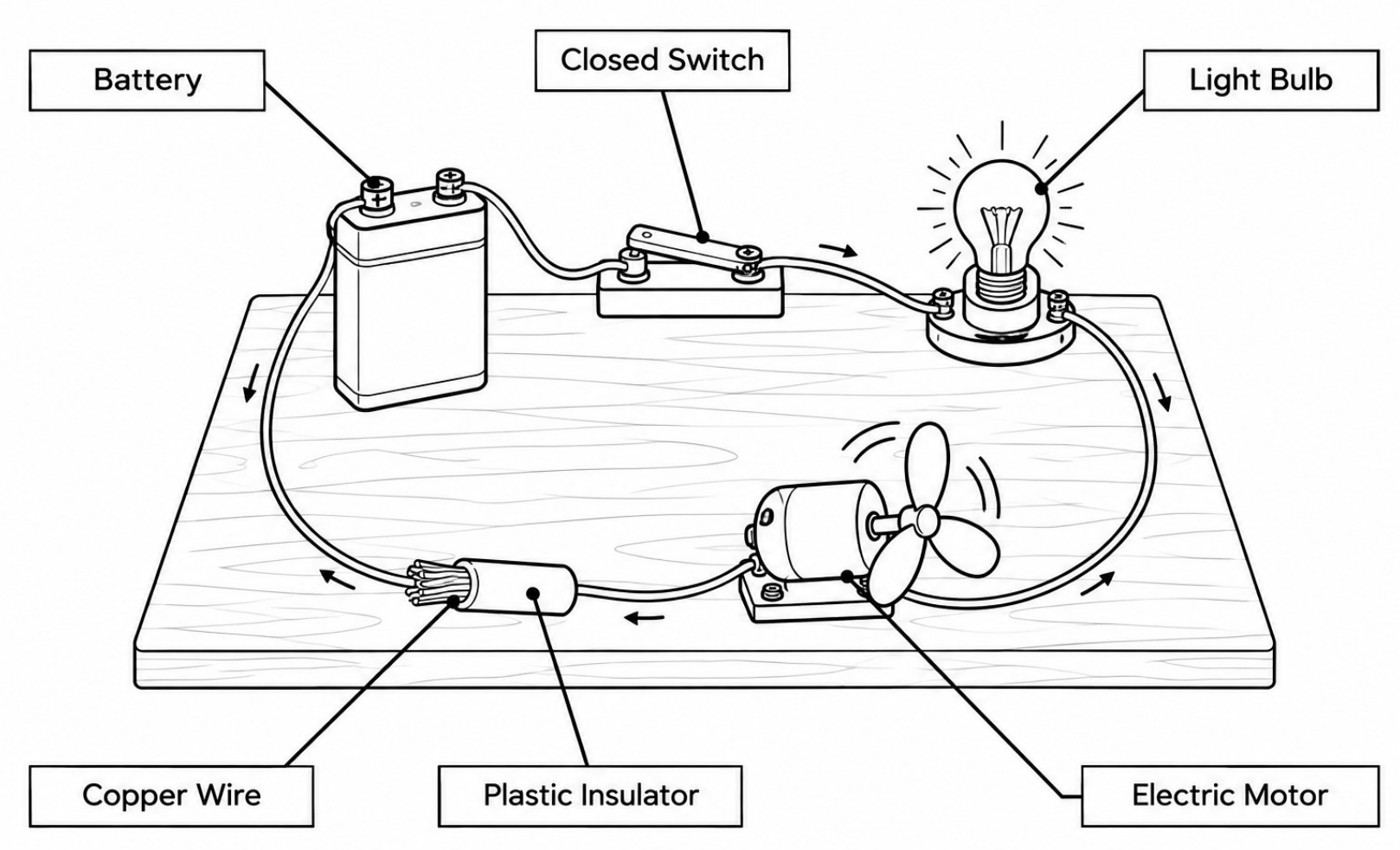

Complete Electrical Circuit

